

CCC  
AES Amsterdam  
March 2003

# Audio-frequency shield current induced noise is negligible

(as long as it does not flow in the 0V system)



Eur Ing Keith Armstrong CEng MIEE MIEEE  
phone: +44 (0)1457 871 605 fax: +44 (0)1457 820 145  
keith.armstrong@cherryclough.com

Presented at the Tutorial session "Grounding and Shielding" chaired by Tony Waldron, at the Audio Engineering Society's 114th Convention, Amsterdam, March 23rd 2003

CCC

## Contents

- Audio benefits from EMC installation techniques
- The origin of CM noise in a system
- What to do with the shields of balanced cables ?
- Noise coupling in balanced cables
- Implications for signal/noise ratios
- System CM noise and improved bonding
- Always connect shields to chassis

CCC  
AES Amsterdam  
March 2003


## Audio benefits from EMC installation techniques

- To meet the EMC directive, a number of large pro-audio systems have followed IEC 61000-5-2
  - with cable shields connected to chassis at both ends
    - ♦ allowing 'ground loop' currents to flow in the shields
- These systems have been excellent for EMC
  - but have also been found to have improved audio performance over precious systems (S/N, bandwidth)
- This short presentation helps to explain why the audio performance is so good

CCC
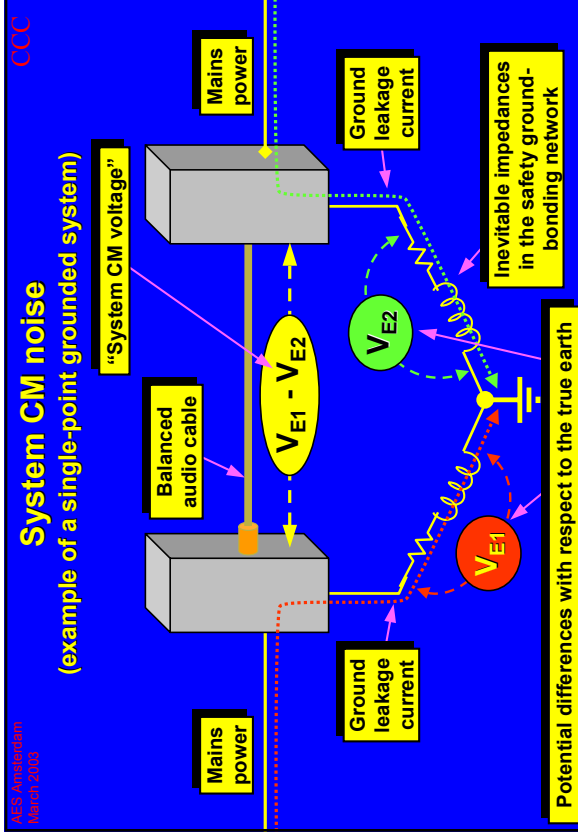
## The origin of common mode (CM) noise in a system


- Systems have a number of items of equipment located in different places
  - so experiencing different ground (earth) potentials from each other
  - and interconnected by balanced shielded cables
- The balanced interconnect is intended to reject the "system CM noise"
  - ♦ the noise voltage that exists between the grounds of two items of interconnected equipment
  - but nothing is perfect


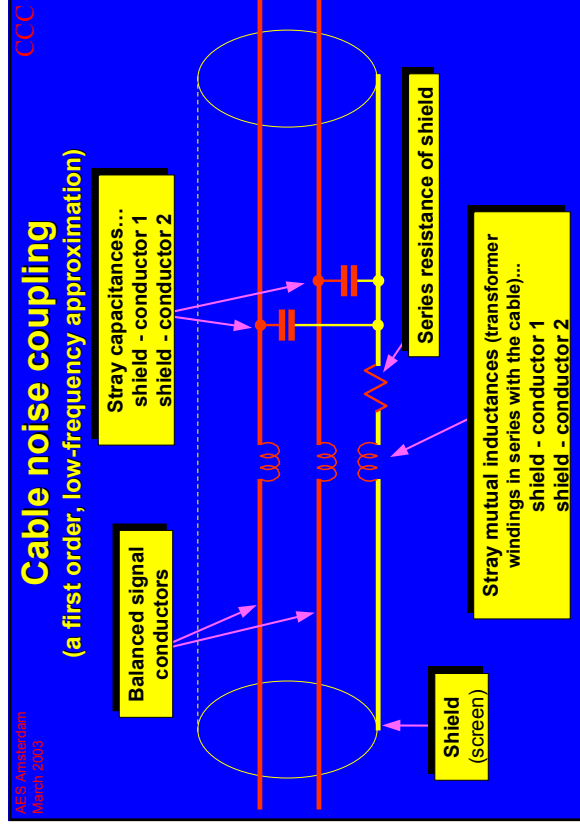
## How should we connect the shield of the balanced cable?

- We can choose to connect each cable's shield to the equipment at one end only, or at both ends
- Experience shows that good EMC performance and low levels of RF demodulation
  - ◆ and compliance with the EMC Directive (EN 55103-1 / -2)
    - is most easily achieved at lowest cost by direct (DC) shield bonding at *both ends*
    - ◆ as recommended by IEC 61000-5-2
  - but how does this affect the amount of system CM noise that gets into the signal?


- **The system noise voltage couples from the shield to the signal conductors by...**
  - **Stray capacitance, which causes a common-mode (CM) noise voltage**
    - and the *imbalance* between the stray capacitances causes differential-mode (DM) noise voltage
  - **Stray mutual inductance**
    - ◆ i.e. a 1:1:1 transformer (above some frequency)
      - causes a CM noise voltage (180° to capacitance noise)
      - and the *imbalance* between the stray mutual inductances causes a DM noise voltage



KEB Armstrong  
March 2003
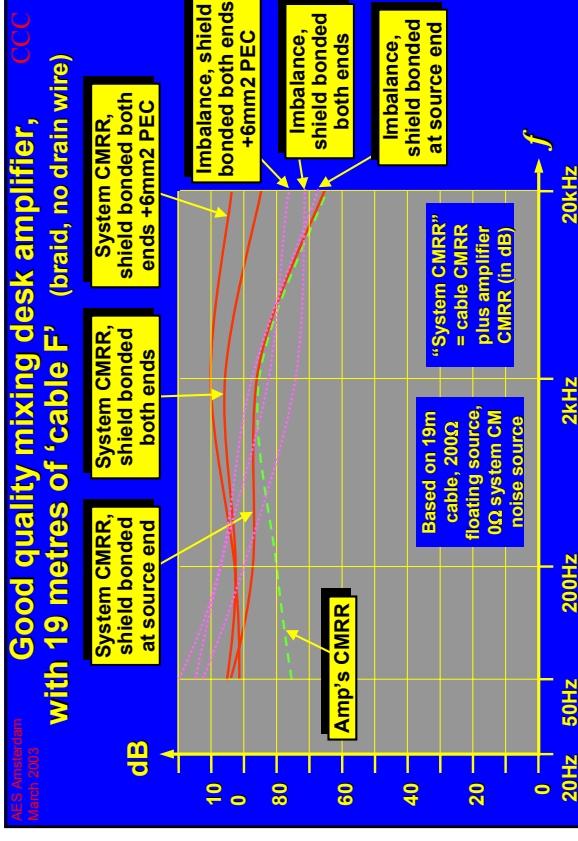
## Implications for signal/noise (S/N) ratios


- **The CM voltage on both of the signal conductors**
  - is processed by the amplifier's CMRR and its gain, resulting in a DM noise
- **The imbalance (DM) voltage between the signal conductors**
  - is processed by amplifier gain as if it is wanted signal
- **Here are some examples for a cable type "F"**
  - showing the relative effects of each of the above noise contributions....



KEB Armstrong  
March 2003
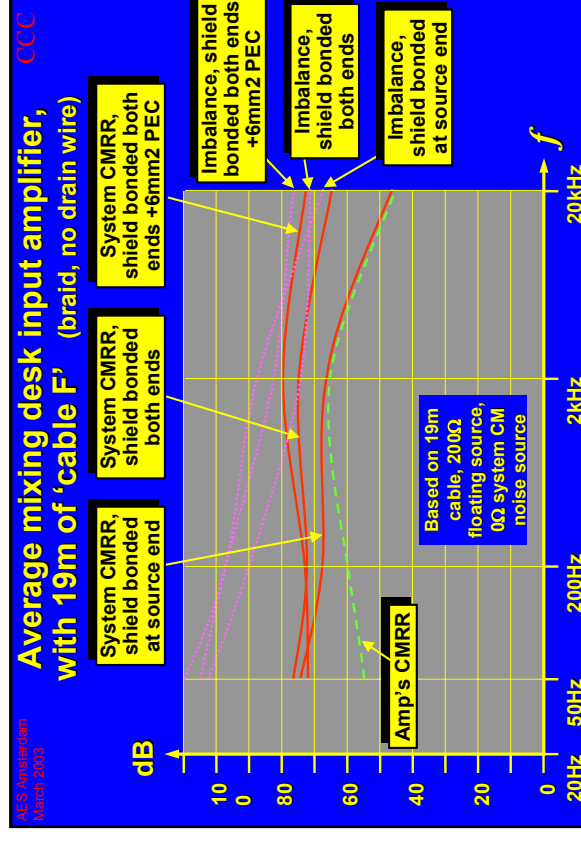
## 19m of 'cable F' with a good mixing desk amplifier

- **Single-ended shield bonding at source**
  - gives better system CM noise than would be expected from the amp's CMRR spec, below 2kHz
- **Bonding shield at both ends makes system CM noise worse by up to 15dB above 300Hz**
  - achieving >70dB overall, over the frequency range
- **Both-ends-bonded plus 6mm<sup>2</sup> PEC makes system CM noise worse by up to 4dB above 1kHz**
  - achieving >75dB overall, over the frequency range



Keith Armstrong  
March 2003

## 19m of 'cable F' with an average mixing desk amplifier

CCC

- Single-ended shield bonding at source
  - gives better system CM noise than would be expected from the amp's CMRR spec, below 2kHz
- Bonding shield at both ends makes system CM noise better by up to 19dB, above 50Hz
  - achieving >65dB overall, over the frequency range
- Both-ends-bonded + 6mm<sup>2</sup> PEC makes system CM noise better by up to 28dB above 100Hz
  - achieving >70dB overall, over the frequency range


Keith Armstrong  
March 2003

## But the system's voltage noise source does *not* have a 0Ω impedance

(as the previous graphs assumed)

CCC

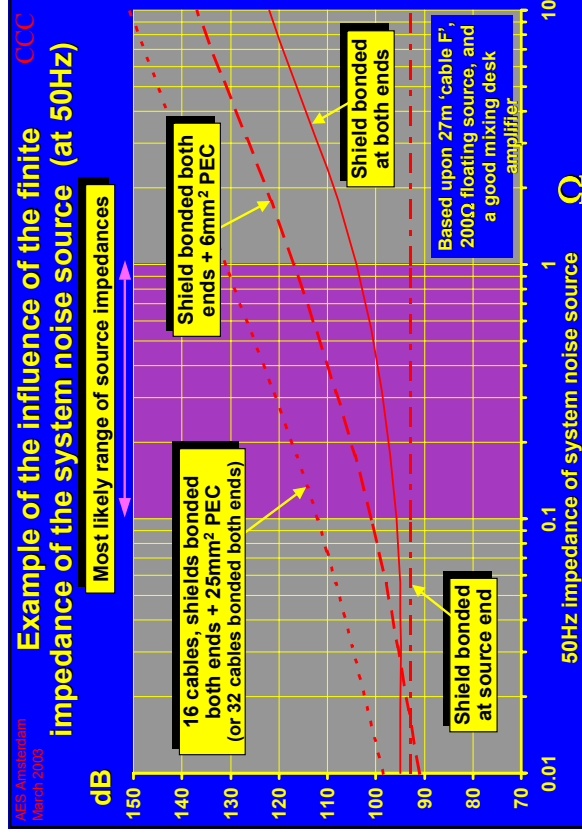- So bonding shields at both ends will *reduce the source noise voltage*
  - as will using PECs
- Reducing both capacitive and inductive coupled cable noise (CM and DM)
- In a large system there can be >100 cables
  - and bonding all their shields at both ends has a very beneficial effect indeed on system CM noise rejection



Keith Armstrong  
March 2003

## Always connect the shield to the chassis, frame or enclosure shield

CCC

- It used to be common to connect shields to circuit 0V
  - now well-known to be very bad practice
  - because of 'common-impedance coupling'
- If the circuit's 0V reference is pure clean water...
  - then the shields are sewers
  - and their currents should never flow in the 0V

KEITH ARMSTRONG  
March 2003

**Why we don't let shield currents flow in the 0V any more**

- Example: a 0.1" wide 0V trace just 1" long (in a 1oz copper printed circuit board)
  - has an impedance of 4.8mΩ at 50Hz
- Just 25mV of 'system CM noise' at 50Hz creates a shield current of 100mA (in 19 metres of 'cable F')
- If this 100mA shield noise current was allowed to flow in the 1" long 0V trace...
  - it would create 480μV of 'common impedance noise' in the circuit's 0V reference system

CCC

KEITH ARMSTRONG  
March 2003

**For a singer or violinist using a typical 200Ω dynamic microphone...**

- 480μV of noise in the 0V could result in a S/N ratio of 20dB
  - worse, where a number of signals share the noisy 0V
- Whereas S/N due to shield-coupled noise alone
  - would be 56dB for an average mixing desk amplifier, and 76dB for a good one (single cable, 0Ω noise source)
  - both much lower than the acoustic background noise for a microphone signal
    - ♦ for 16 cable shields in parallel: >66dB and >86dB likely

CCC

KEITH ARMSTRONG  
March 2003

**Audio-frequency shield current induced noise is negligible**

(as long as it does not flow in the 0V system)

**the end**

**Cherry Clough**  
C O N S U L T A N T S



Eur Ing Keith Armstrong CEng MIEE MIEEE  
phone: +44 (0)1457 871 605 fax: +44 (0)1457 820 145  
keith.armstrong@cherryclough.com

CCC


KEITH ARMSTRONG  
March 2003

**Some additional useful material follows.....**

CCC

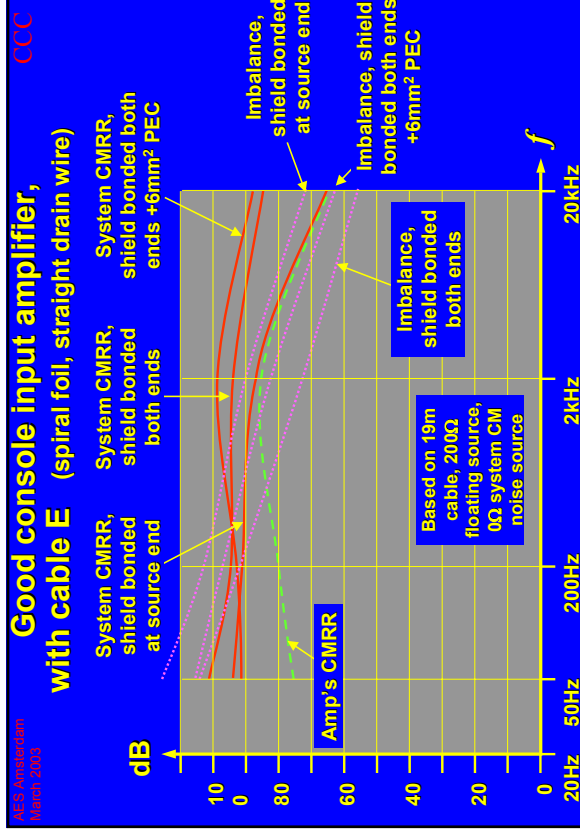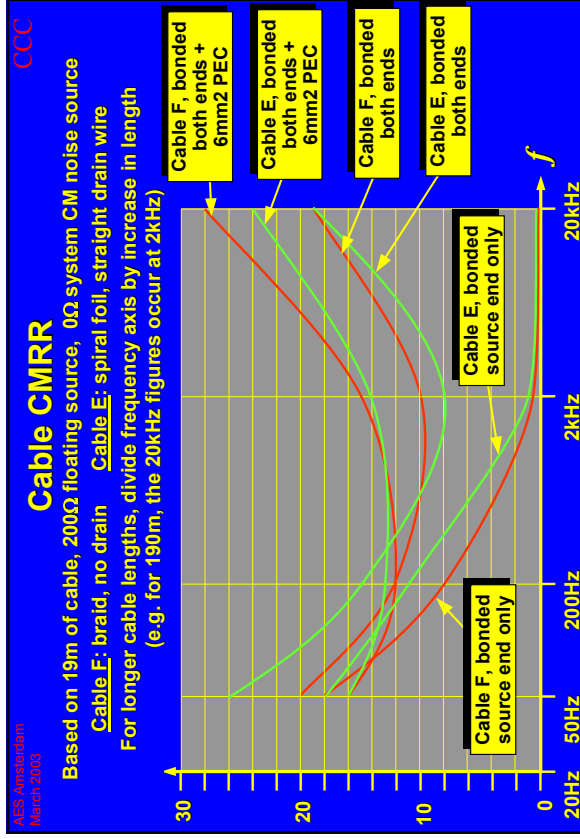

- **19m of cable E with a good console amplifier**
  - gives better system CM noise than would be expected from the amp's CMRR spec, below 2kHz
  - **Bonding shield at both ends makes system CM noise worse by up to 15dB above 200Hz**
    - giving >70dB overall, over the frequency range
  - **Both-ends-bonded plus 6mm² PEC makes system CM noise worse by up to 5dB above 1kHz**
    - giving >75dB overall, over the frequency range

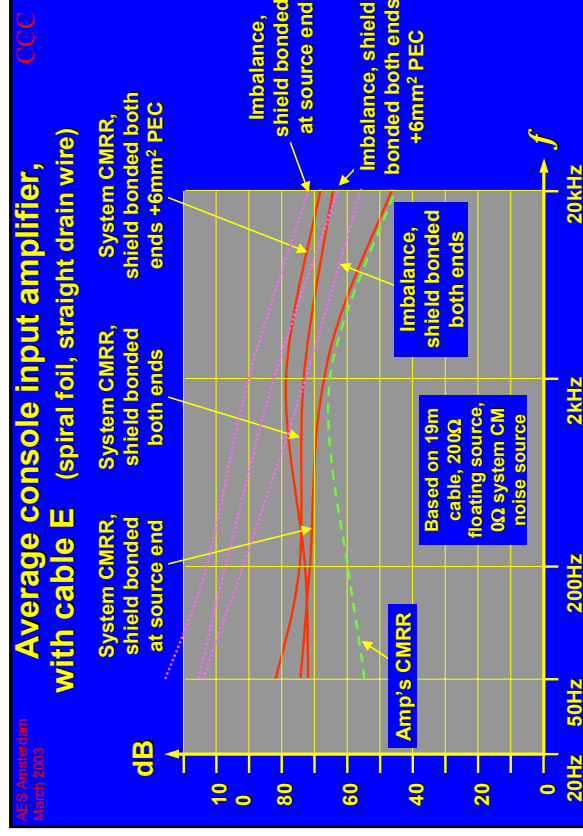

CCC  
19m of cable E  
with an average console amplifier

- **Single-ended shield bonding at source**
  - gives better system CM noise than would be expected from the amp's CMRR spec, below 2kHz
- **Bonding shield at both ends makes system CM noise better by up to 10dB, above 200Hz**
  - giving >55dB overall, over the frequency range
- **Both-ends-bonded + 6mm<sup>2</sup> PEC makes system CM noise better by up to 18dB above 50Hz**
  - giving >62dB overall, over the frequency range